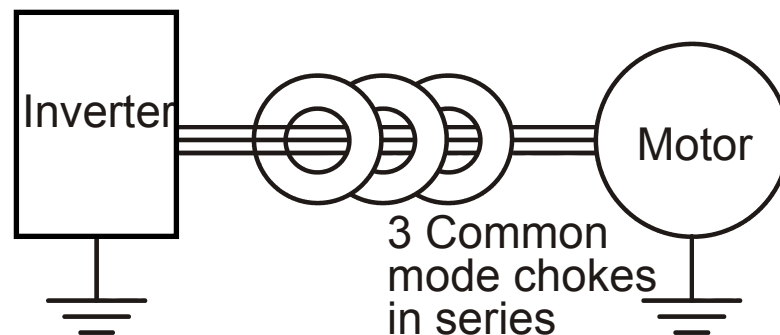



Scaling Issues for Common Mode Chokes to Mitigate Ground Currents in Inverter-Based Drive Systems

Annette Muetze

Electrical and Computer Engineering
University of Wisconsin-Madison, USA




Source: Magnetec GmbH

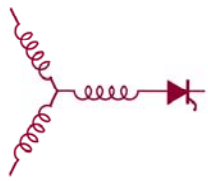


Outline

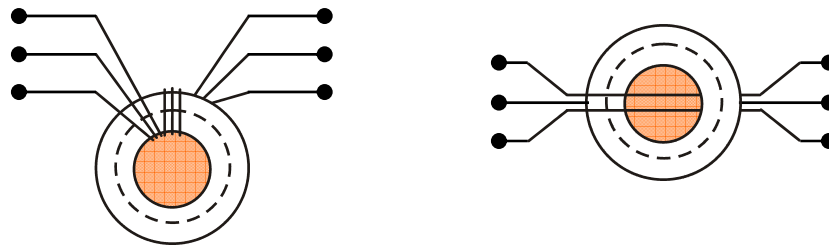
- Motivation
 - ...to use common mode chokes in the inverter-output → requirements?
- Influence of the Inductance Value on the Current Reduction
 - Equivalent circuit, general case and un-damped case
- Physics of Common Mode Chokes
 - Fundamentals, wound and feed-through chokes



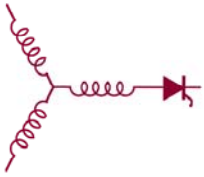
- Design Criteria
 - Window area, current-to-diameter ratio, minimum diameter,...
- Measurement Results
- Summary



Motivation

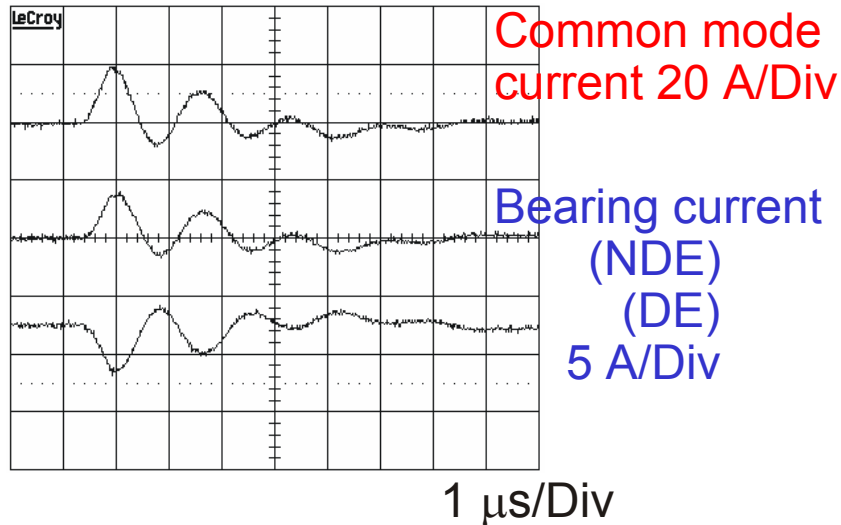


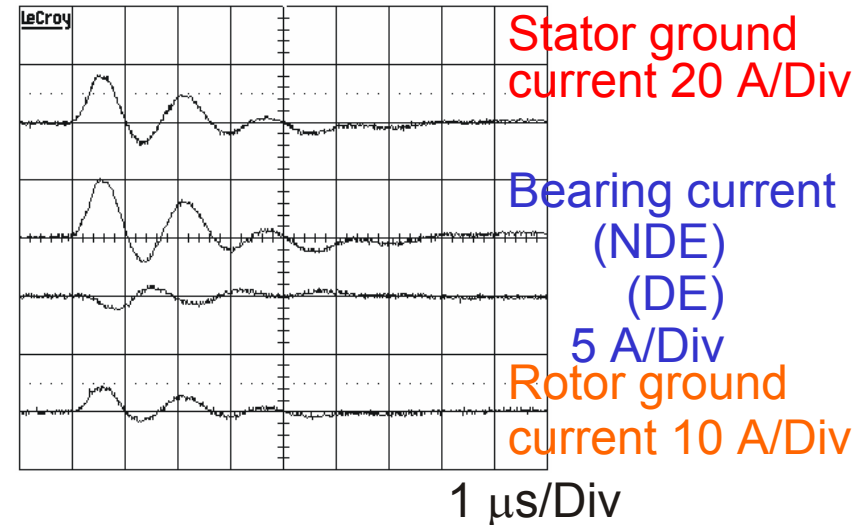
Circulating bearing currents
motor speed $n = 3000$ /min



Bearing currents due to rotor ground currents,
motor speed $n = 15$ /min, rotor grounded on DE-side

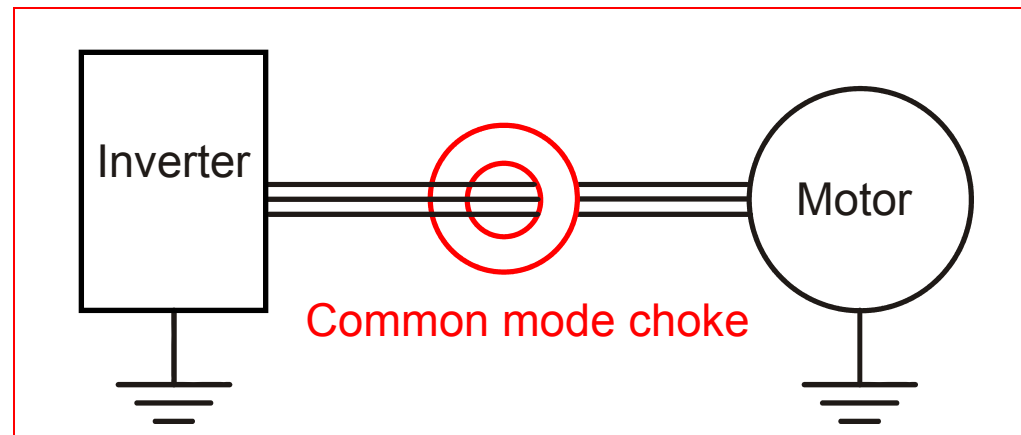Squirrel-cage induction motor, frame size 400 mm, 500 kW rated power, bearing temperature $T_b \approx 70^\circ\text{C}$ (Measurements were obtained in the frame of a research project at Darmstadt University of Technology, Institute of Prof. Binder)



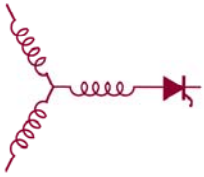




Modeling: Lumped Parameter Circuit


▷ Approach:

RLC-Circuit (L : function of cable, R and C : function of motor)
[Ogasawara, Akagi, 1996]

▷ The peak HF common mode current amplitude is searched for:
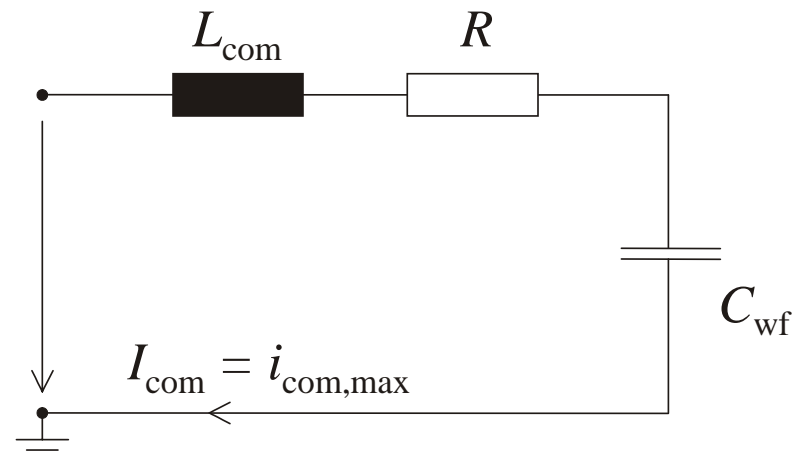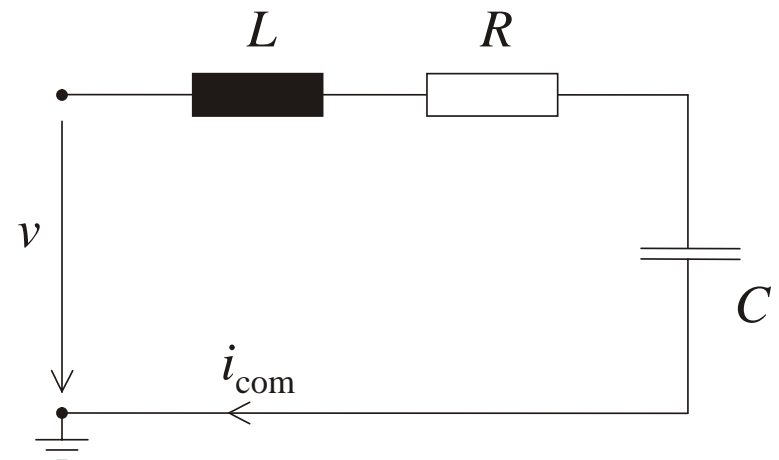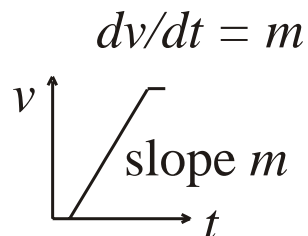
$$I_{\text{com}} = f\left(\frac{v_{\text{Lg}}}{dt}, L_{\text{com}}, C_{\text{wf}}\right) = f(m, L_{\text{com}}, C_{\text{wf}})$$




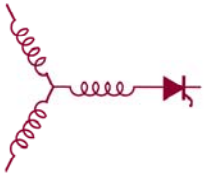

Lumped Parameter Circuit: Parameters

Common mode inductance
... required value ...???

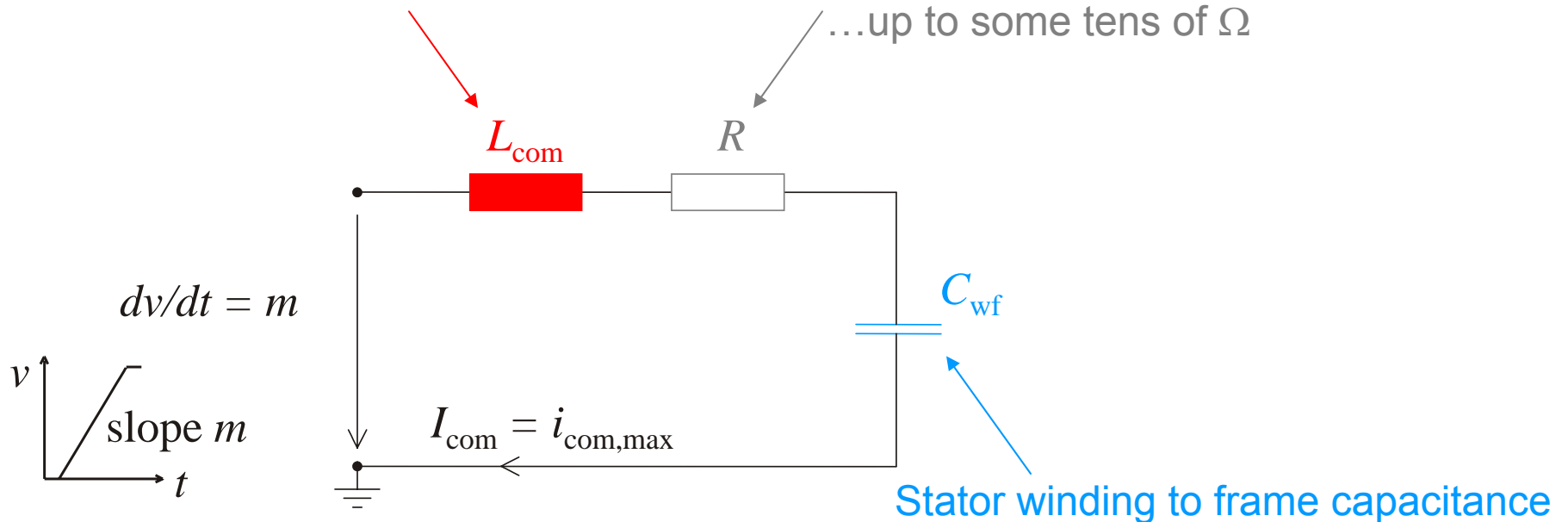
Related to the motor only
Damping due to motor frame resistance
including skin effect;
...up to some tens of Ω



► Assumptions:

- short motor leads ($L_{cable} \approx 0$)
- $I_{com} = i_{com,max}$ occurs during rise time t_r

All values are per phase values.

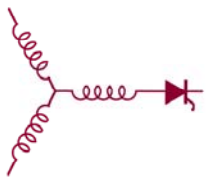

Influence of L_{com} on the Current Reduction: Problem Formulation

▷ $i_{\text{com}}(t) = f(m, L_{\text{com}}, C_{\text{wf}})$

▷ $i_{\text{com}}(t) = f(\omega_0, Z_0, \xi)$


where $\omega_0 = \sqrt{\frac{1}{L_{\text{com}} C_{\text{wf}}}}$ $Z_0 = \sqrt{\frac{L_{\text{com}}}{C_{\text{wf}}}}$ $\xi = \frac{R}{2} \sqrt{\frac{C_{\text{wf}}}{L_{\text{com}}}}$

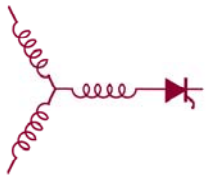1. Under-damped case
2. Critically-damped case
3. Over-damped case





$i_{\text{com}}(t) = \dots \rightarrow I_{\text{com}} = f(m, L_{\text{com}}, C_{\text{wf}}) = f(\omega_0, Z_0, \xi) \dots$





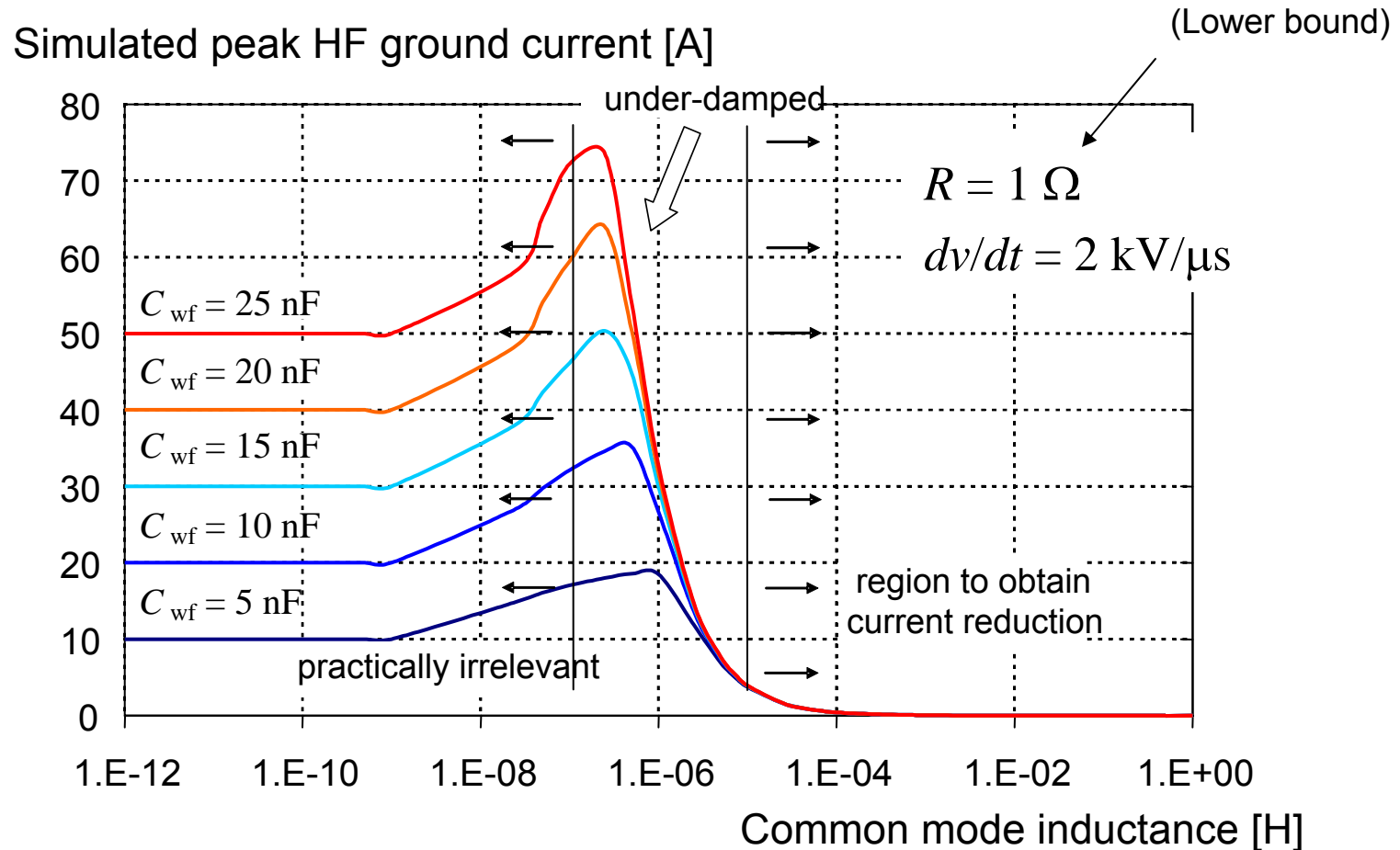
Influence of L_{com} on the Current Reduction: General Case




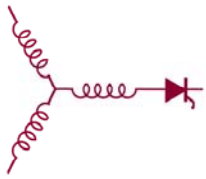

Influence of L_{com} on the Current Reduction: General Case cont.

Simulated peak HF ground current [A]

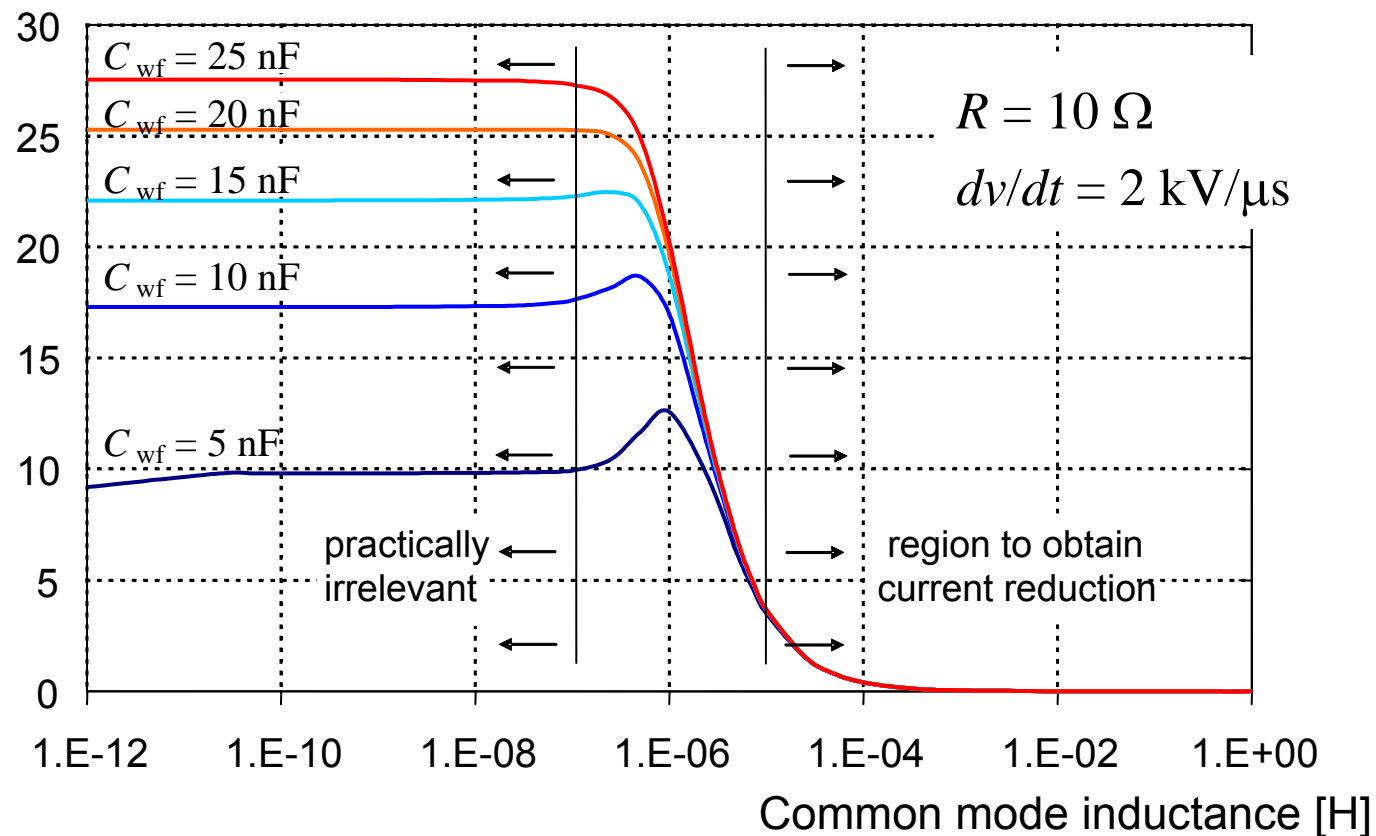

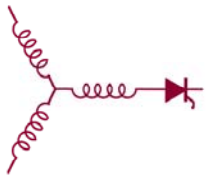


Influence of L_{com} on the Current Reduction: Un-damped Case

▷ $i_{\text{com}} = mC_{\text{wf}}\{1 - \cos(\omega_e t)\}$


▷ $I_{\text{com}} = 2mC_{\text{wf}}$

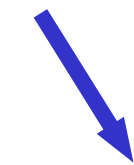
Minimum value of common mode inductance [uH]




$$L_{\text{com}} \geq L_{\text{com,min}} = \frac{1}{C_{\text{wf}}} \left(\frac{t_r}{\pi} \right)^2$$


$$t_r = \frac{T}{2}$$

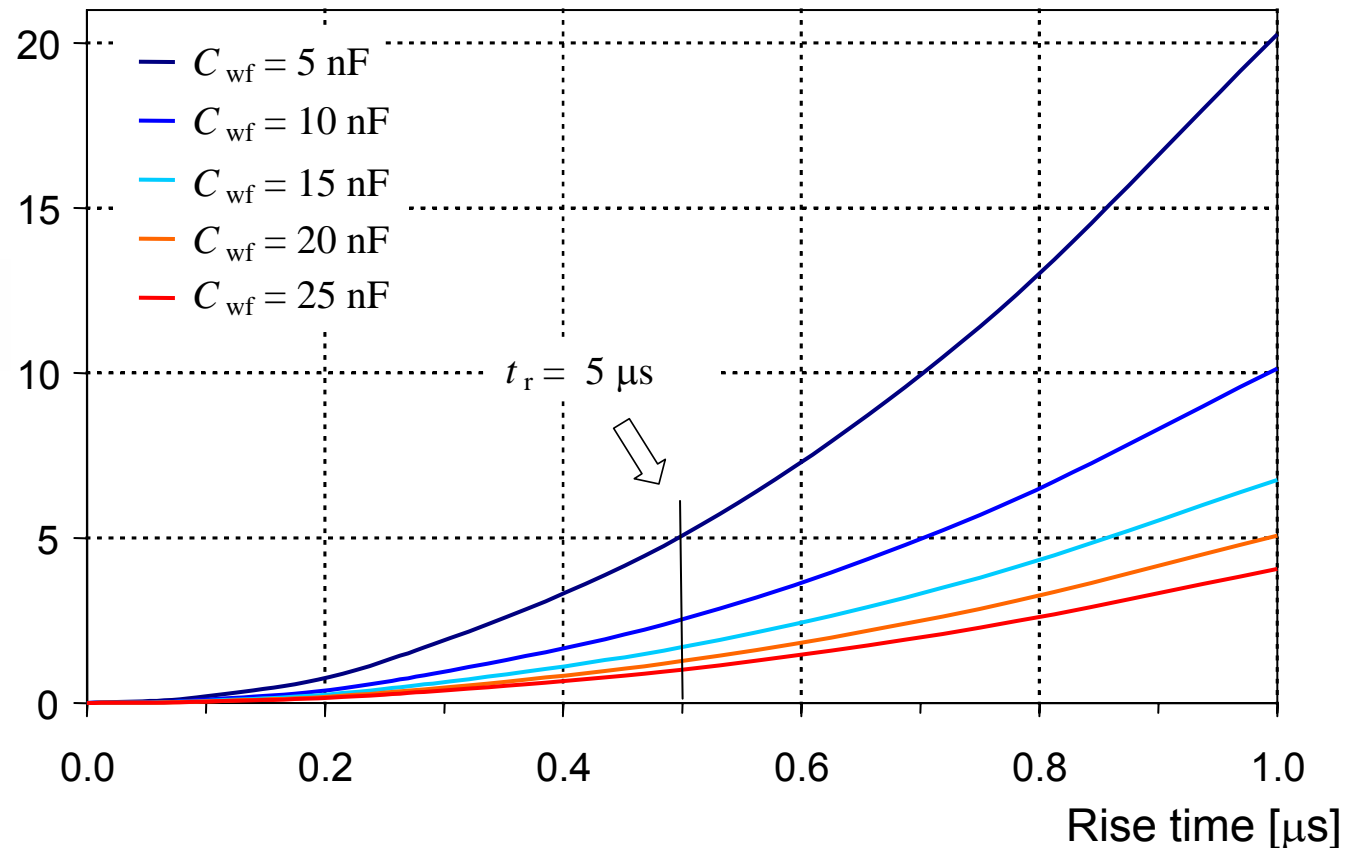

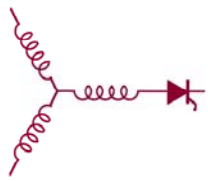


Outline

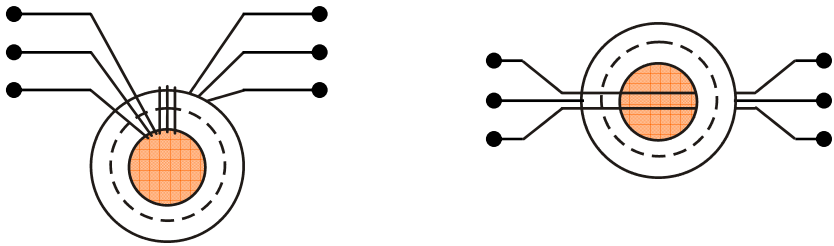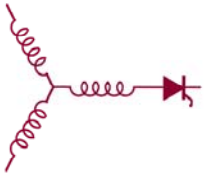- Motivation
 - ...to use common mode chokes in the inverter-output → requirements?
 - Influence of the Inductance Value on the Current Reduction
 - Equivalent circuit, general case and un-damped case
 - Physics of Common Mode Chokes
 - Fundamentals, wound and feed-through chokes
- 
- Design Criteria
 - Window area, current-to-diameter ratio, minimum diameter,...
 - Measurement Results
 - Summary



Physics of Common Mode Chokes


Wound choke:

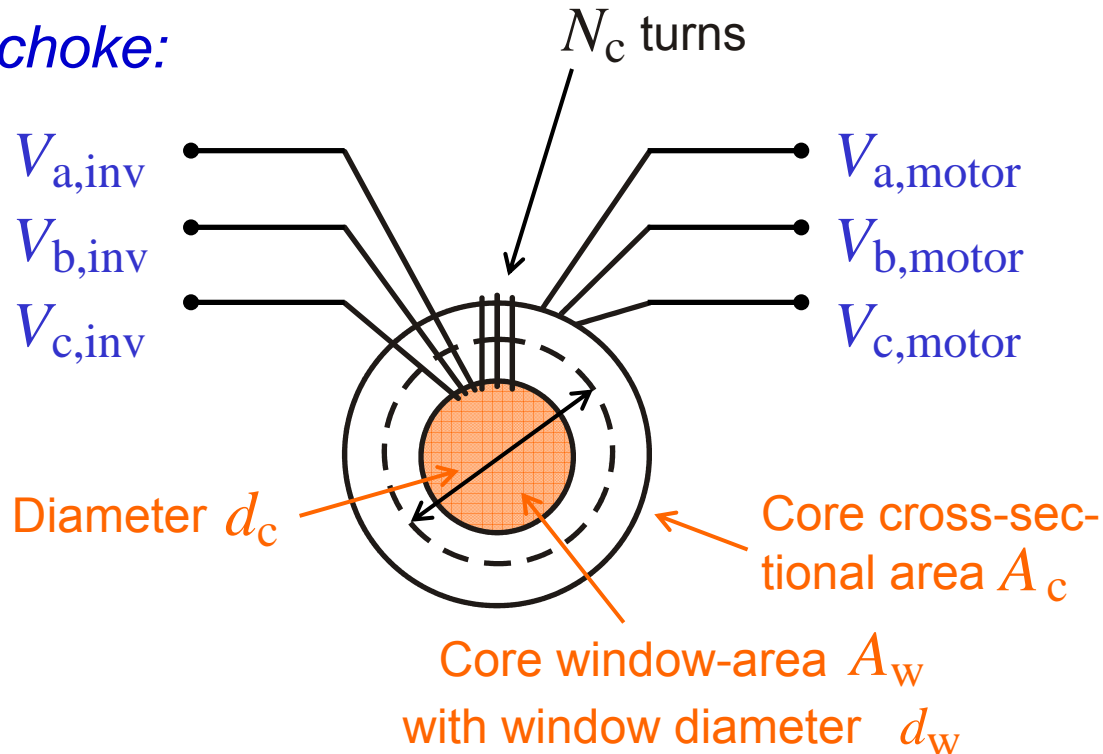

Inductance value:


$$L_{\text{com}} = \frac{N_c^2 \mu A_c}{\pi d_c}$$

(Un-gapped cores)

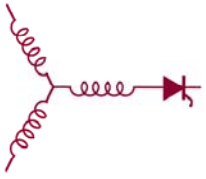


Physics of Common Mode Chokes cont.

Wound choke:

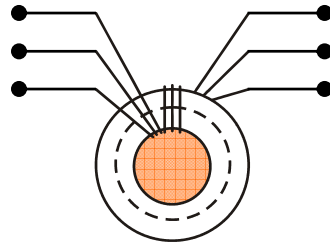

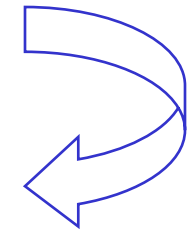
$$L_{\text{com}} = \frac{N_c^2 \mu A_c}{\pi d_c}$$




$$N_c = 1$$

Feed-through choke:

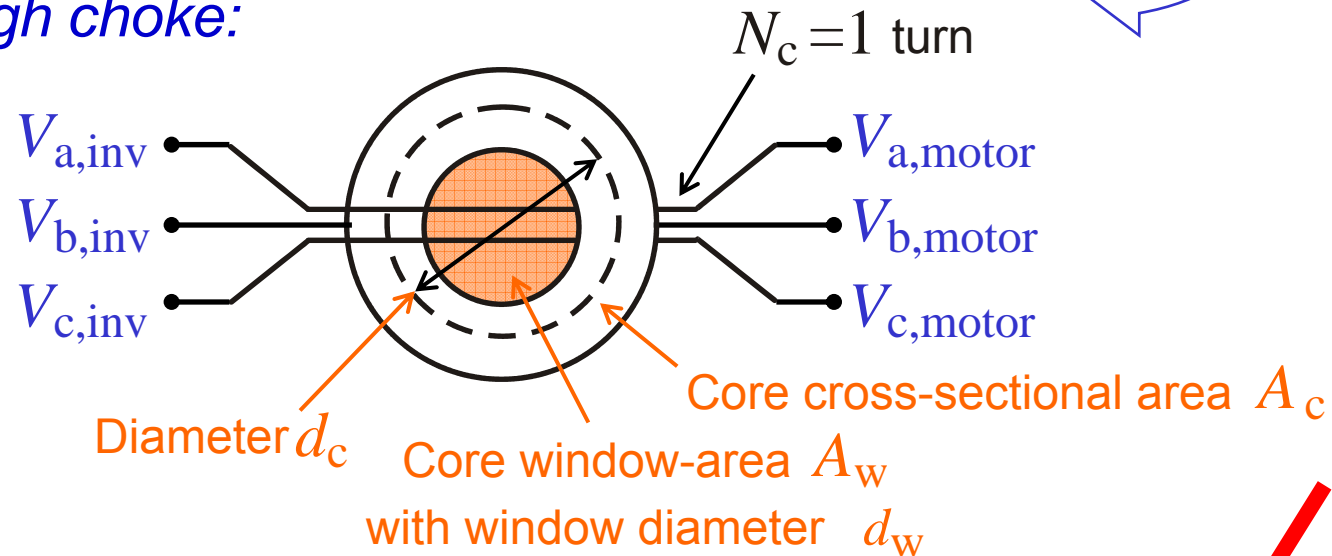


Inductance value:

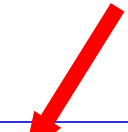



$$L_{\text{com}} = \frac{\mu A_c}{\pi d_c}$$

(Un-gapped cores)

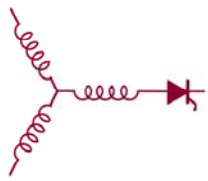


Outline

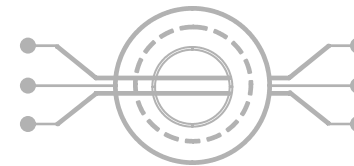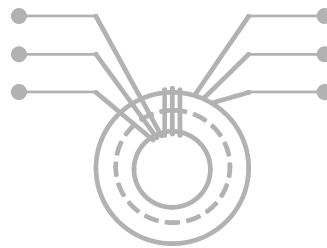- Motivation
 - ...to use common mode chokes in the inverter-output → requirements?
- Influence of the Inductance Value on the Current Reduction
 - Equivalent circuit, general case and un-damped case
- Physics of Common Mode Chokes
 - Fundamentals, wound and feed-through chokes



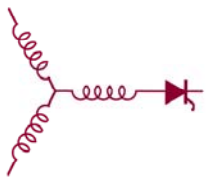- Design Criteria
 - Window area, current-to-diameter ratio, minimum diameter,...
- Measurement Results
- Summary



Accommodation of the Motor Leads


Minimum core window area and bore of feed-through toroidal cores for different cable cross-sectional areas:

$$N_c = 1, k_w = 0.4$$

| Cable cross-sectional area | Current carrying capability per individual cable ^{*)} | Core minimum window area | Core minimum bore diameter |
|----------------------------|--|--------------------------|----------------------------|
| 70 mm ² | 207 A | 525 mm ² | 26 mm |
| 150 mm ² | 335 A | 1125 mm ² | 38 mm |
| 300 mm ² | 523 A | 2250 mm ² | 54 mm |


More than a factor of 2 smaller than the minimum bore diameter to avoid saturation! – Already at 1 turn!

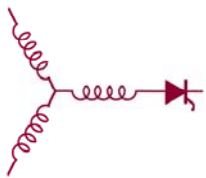
^{*)} At 30°C ambient temperature, according to DIN VDE 0276 Part 1000



Maximum d_c/I_{com} – Ratio for Avoiding Core Saturation
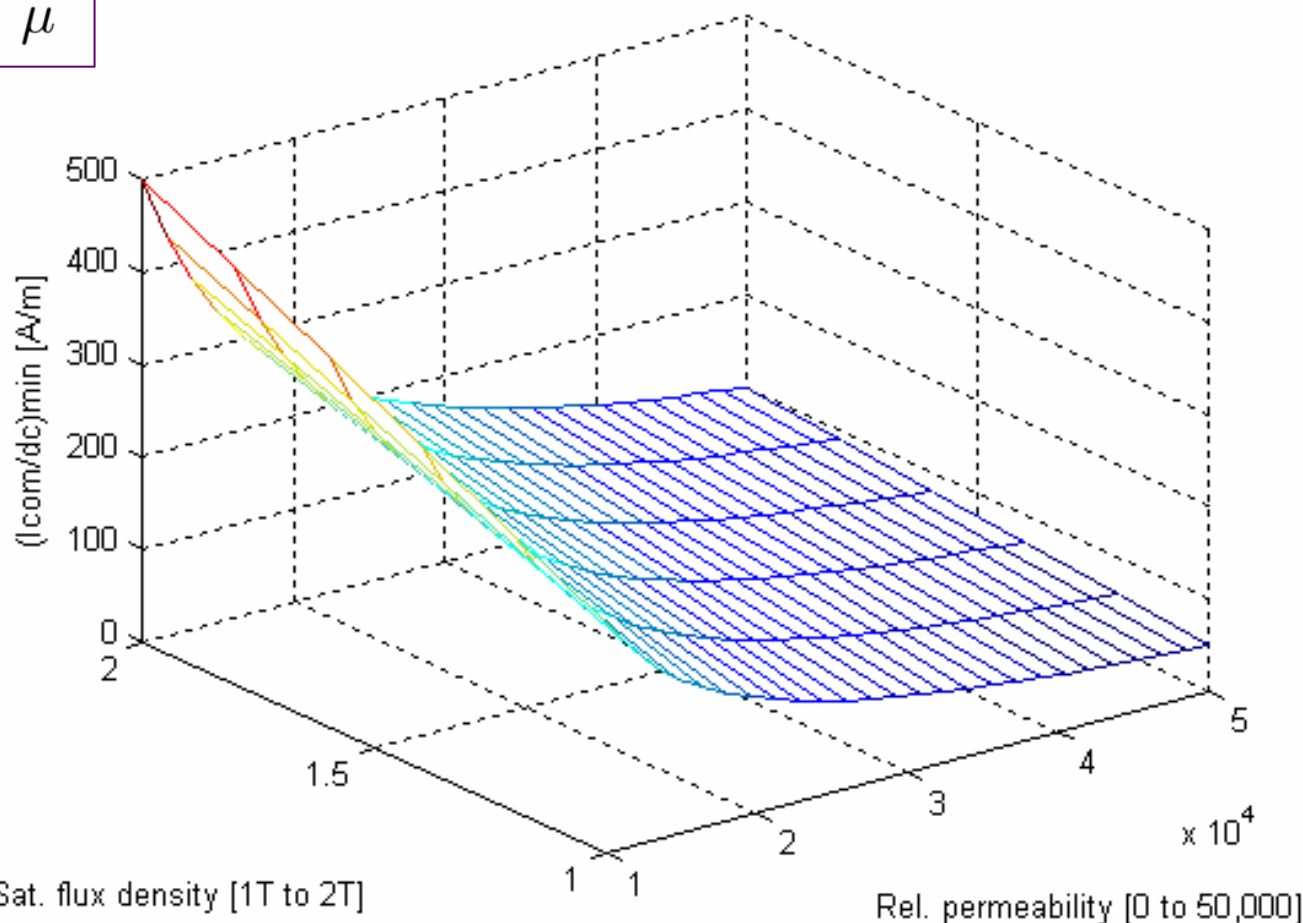
$$\left\{ \frac{I_{com}}{d_c} \right\}_{max} = \frac{\pi}{N_c} \frac{B_s}{\mu}$$




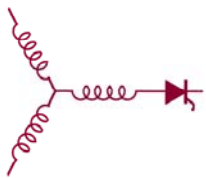


Minimum Core Diameter for Avoiding Core Saturation

$$d_{c,\min} = \frac{I_{\text{com}} 4\pi 10^{-7} \mu_r}{B_s}$$

High value
by intention

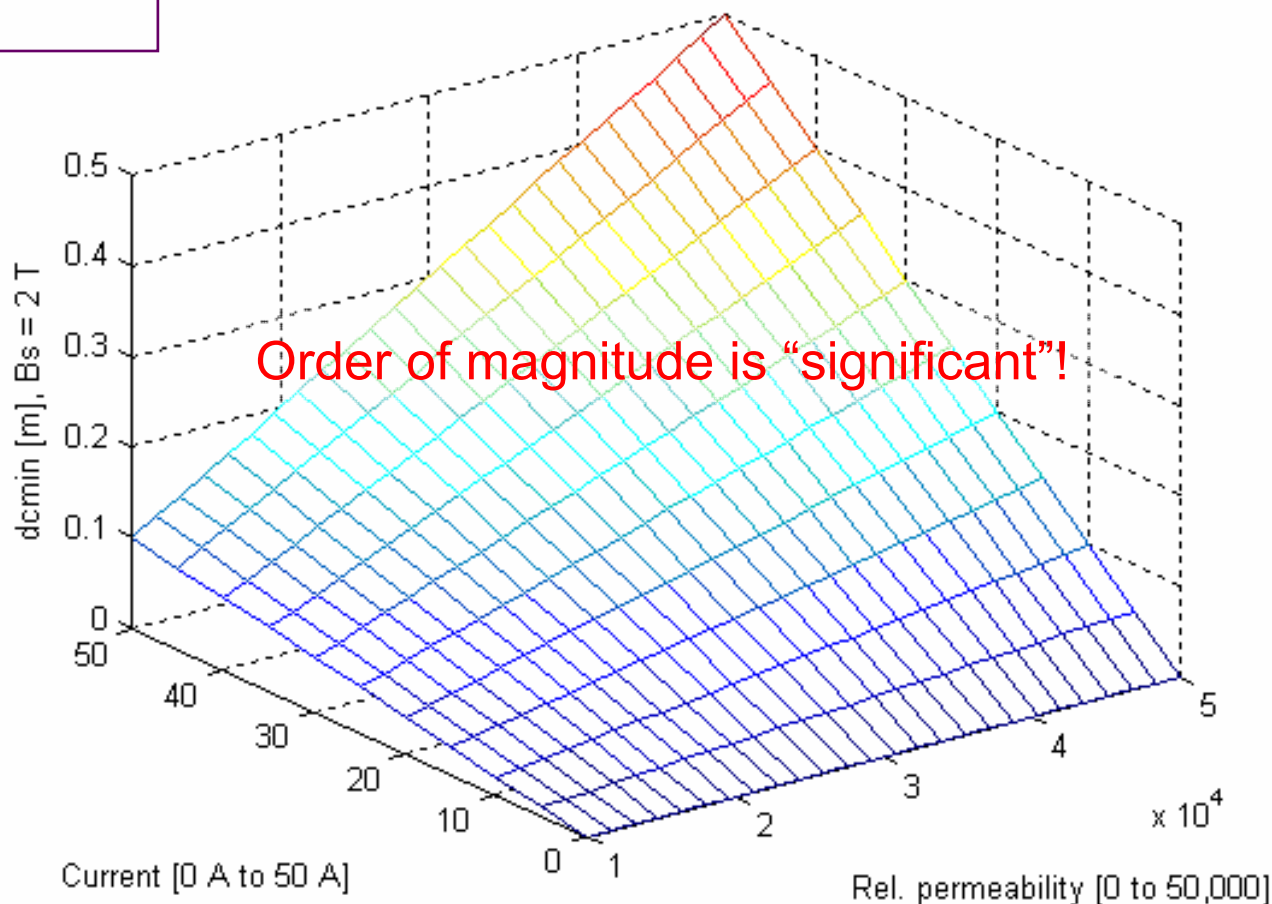


(Un-gapped cores)

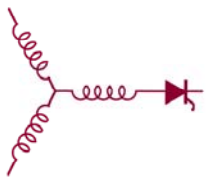


Cross Sectional Area as Function of L_{com}

Core cross sectional area [mm^2]

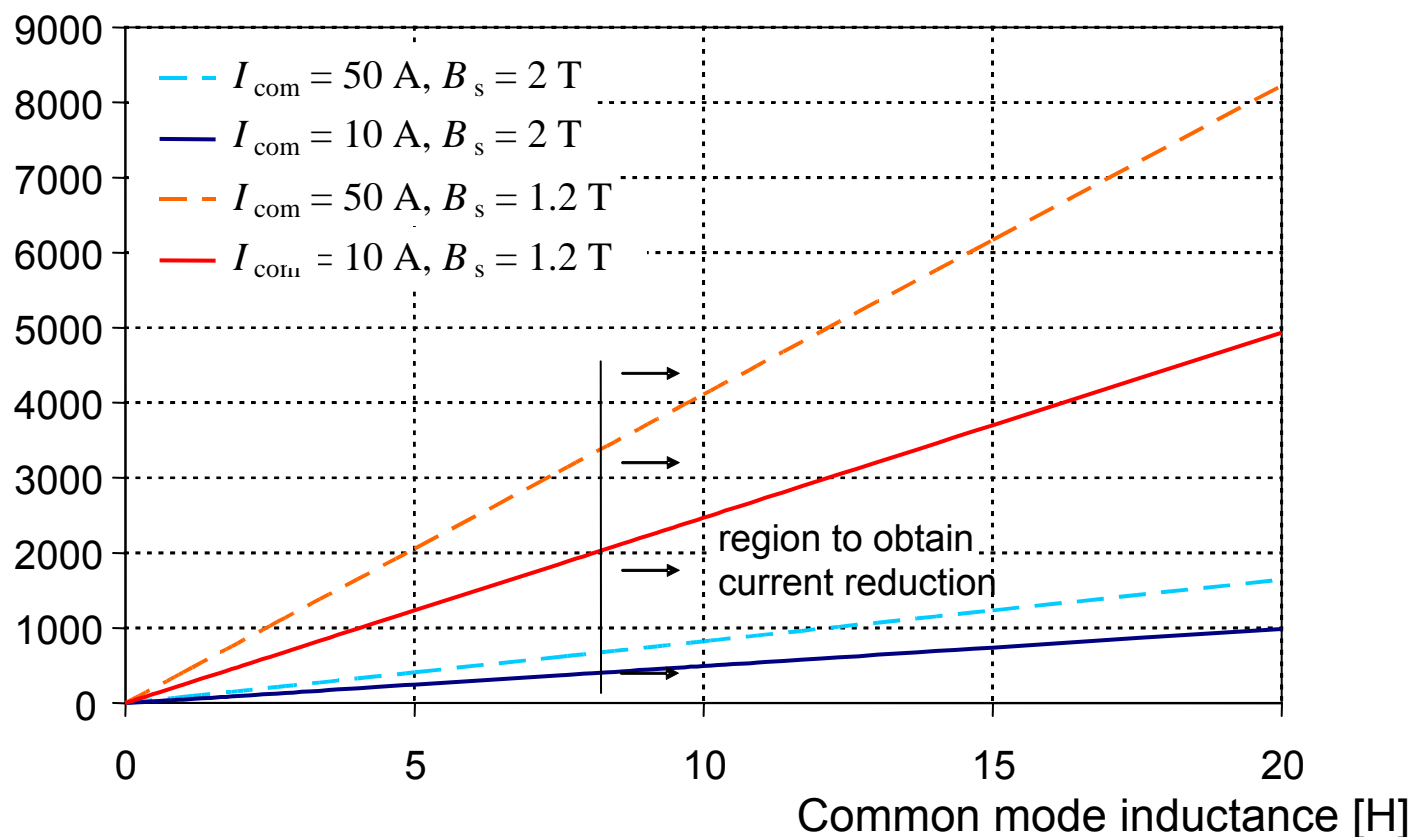



(Un-gapped chokes, constant μ)

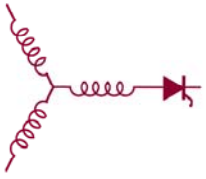

Use of Several Feed-Through Cores in Series

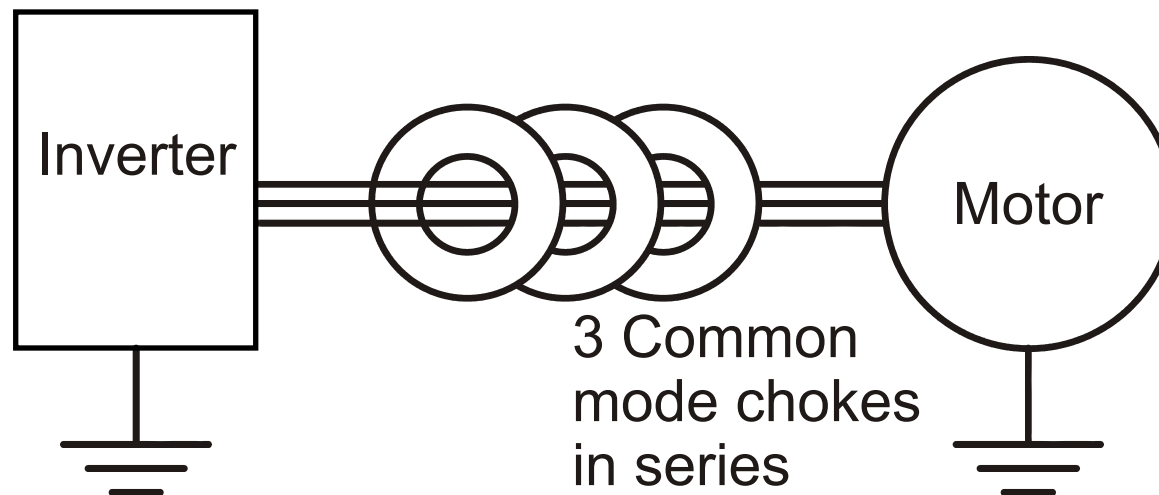
- ▷ Large cross sectional area required to achieve L_{com}
- ▷ Increase of the N_c not an option because of saturation
 - ▷ Use several cores in series



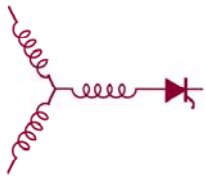


Outline

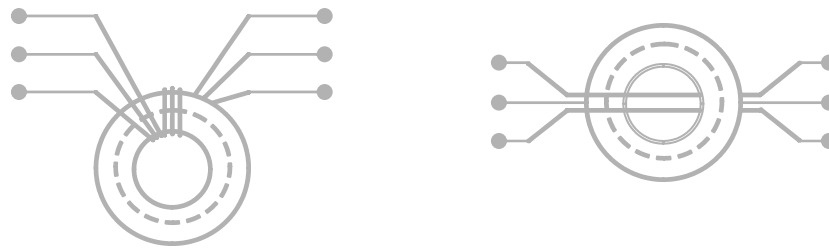- Motivation
 - ...to use common mode chokes in the inverter-output → requirements?
- Influence of the Inductance Value on the Current Reduction
 - Equivalent circuit, general case and un-damped case
- Physics of Common Mode Chokes
 - Fundamentals, wound and feed-through chokes




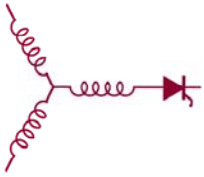
- Design Criteria
 - Window area, current-to-diameter ratio, minimum diameter,...
- Measurement Results
- Summary



Measurement Results

- Commercially available un-gapped toroidal core
("Cool Blue[®]" of Magnetec GmbH)
 - Nano-crystalline material with $\mu_r = 30,000$ (10 kHz)
 - Tabulated inductance (20...30) μH
- Drive with $C_{\text{wf}} = 8 \text{ nF}$, $dv_{\text{Lg}}/dt = 2 \text{ kV}/\mu\text{s}$
 - Reduction of $I_{\text{com}} = 28 \text{ A}$
 - 1 core: by 15%
 - 2 cores: by 36%
- Minimum $d_c = 280 \text{ mm}$
 \approx twice actual value
 - Reduction of the choke performance by $\approx 50\%$
 - Compares well with above Figures

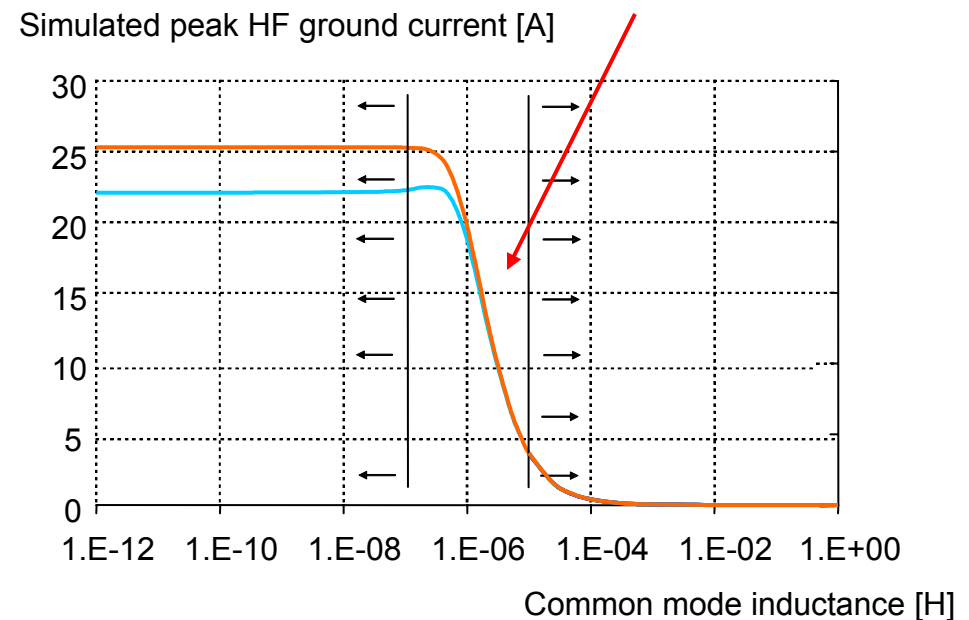

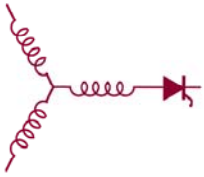

Summary

1. Minimum inductance value of the chokes: in the order of $10 \mu\text{H}$
2. Rather large values of I_{com} require a minimum bore diameter for avoiding saturation that results in a core window area large enough to accommodate the motor leads
3. Any number of turns > 1 will likely result in increased saturation (\rightarrow not improve the choke performance) (Un-gapped cores)
4. Aiming for a higher value of relative permeability than 10,000 is arguable (Un-gapped cores)
5. Use of several cores in series